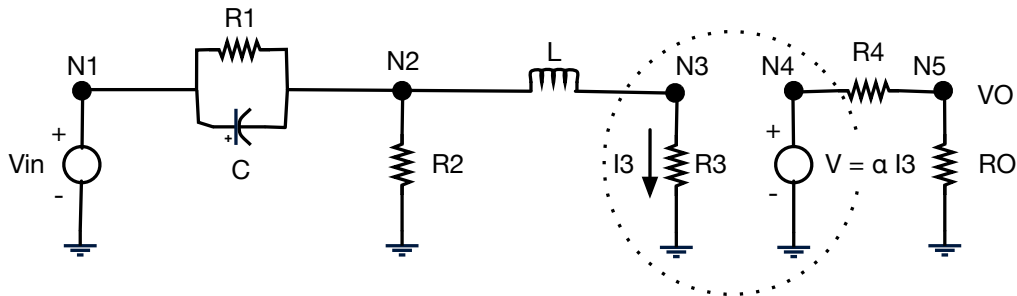


# ELEC 4700 MNA Building

Tom Smy

March 3<sup>th</sup>, 2022. Due March 6<sup>th</sup> @ midnight.

**Goal** In this PA you will do a DC and AC analysis of a linear circuit using MNA techniques. The circuit you will analyze is:



with  $R_1 = 1$ ,  $C = 0.25$ ,  $R_2 = 2$ ,  $L = 0.2$ ,  $R_3 = 10$ ,  $\alpha = 100$ ,  $R_4 = 0.1$  and  $R_O = 1000$ .

## Tasks

### 1. Formulation:

- Write out the 7 differential equations (you might use less or more depending on your formulation) that represent this network in the time domain using KCL ( $\sum I = 0$  at each node). Equations of use:
  - $V = IR$
  - $I = C \frac{dV}{dt}$
  - $V = L \frac{dI}{dt}$  – for the inductor it is useful to declare a new variable  $I_L$
- Now write them in the frequency domain  $\frac{dY}{dt} \rightarrow j\omega Y(\omega)$
- Write down the matrices  $\mathbf{C}$ ,  $\mathbf{G}$ , and the vector  $\mathbf{F}$  that can be used to describe the network using:

$$\mathbf{C} \frac{d\mathbf{V}}{dt} + \mathbf{G}\mathbf{V} = \mathbf{F}$$

or

$$(\mathbf{G} + j\omega\mathbf{C})\mathbf{V} = \mathbf{F}(\omega)$$

### 2. Programing:

- In Matlab create the  $\mathbf{C}$ ,  $\mathbf{G}$  matrices.
- For the DC case sweep the input voltage  $V_1$  from -10V to 10V and plot  $V_O$  and the voltage at  $V_3$ .
- For the AC case plot  $V_O$  as a function of  $\omega$  also plot the gain  $\frac{V_O}{V_1}$  in dB.
- For the AC case plot the gain as function of random perturbations on  $C$  using a normal distribution with  $std = .05$  at  $\omega = \pi$ . Do a histogram of the gain.

**Checkout** When you are finished:

- Create a new repo on your github account called MNPA
- Clone the repo to your machine
- Add your code to the repo, commit, and push it back to github
- Check that it worked, if it did, you're all set